

# I-V Characteristics of Solar Cell

Jahnavi Devangula  
20D070025

September 2022

## 1 Overview of the experiment

### 1.1 Aim of the experiment

To measure the I-V characteristics in forward and reverse bias of the solar cell in the dark and light conditions under two different illuminations. To examine the use of a solar cell as a power source, by measuring the current and voltage across it. Also, measuring the power generated by a solar cell when used in the above operation, by measurement of open-circuit voltage and short-circuit current across the cell.

### 1.2 Methods

In the first part of the experiment, the solar cell was placed in a circuit, and voltage across it was varied. The I-V characteristics was then measured for 3 conditions, i.e., dark, low-light and high-light. LEDs were used inside the black box to generate light.


In the next part, the cell was placed under pre-determined conditions of light, and the current and voltage generated by the solar cell were measured.

In the last part, we place the cell in a similar setup as before, and measured the open-circuit voltage and short-circuit current across it.


## 2 Design
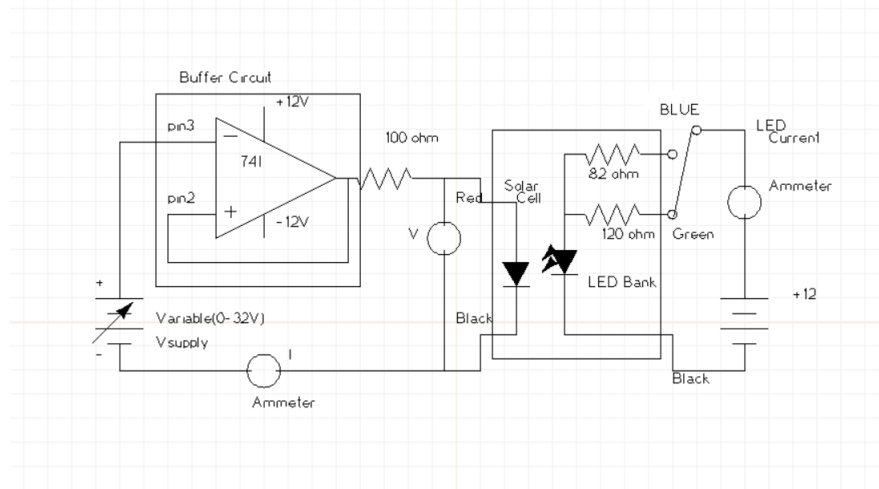
### 2.1 Part 1: Measurement of I-V characteristics

To vary the illumination of LEDs, current through them was varied.


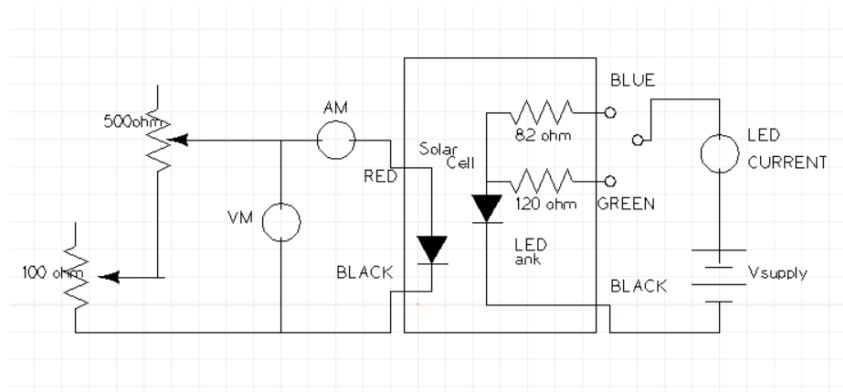
### 2.2 Part:-2 Solar cell as power source




Above circuit is used to find the variation of solar cell as power source by changing the load resistance using two potentiometers of  $500\Omega$  and  $100\Omega$ . Found the values of current and voltage from ammeter and voltmeter from open circuit voltage  $V_{oc}$  to short circuit current  $I_{sc}$  and plotted the power graph also.

Fill Factor of Solar Cell was calculated using:-

$$\text{Fill Factor} = \frac{I_{MP} V_{MP}}{I_{sc} V_{oc}}$$
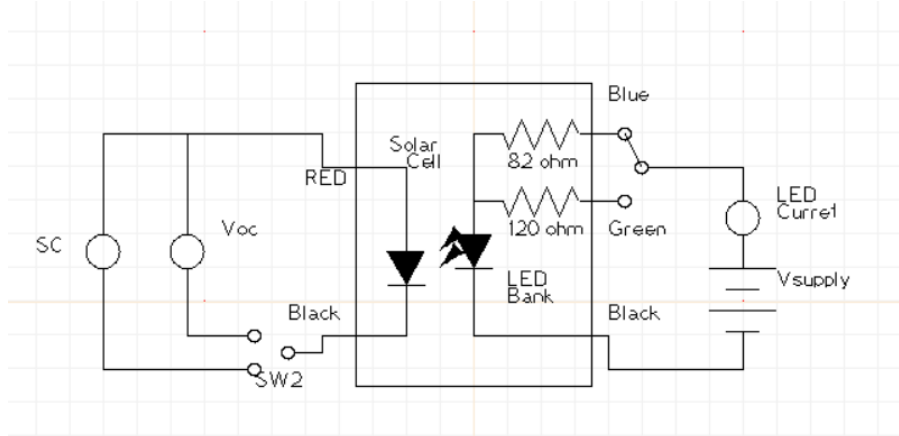
### 2.3 Part:-3 Measurement of $V_{oc}$ and $I_{sc}$ at different illumination levels



In this part we had to measure variation of open circuit voltage  $V_{oc}$  and short circuit current  $I_{sc}$  for different values of LED current by changing supply voltage to Blue LED from  $10mA$  to  $50mA$  in steps of  $10mA$ .

## 3 Simulation results

### 3.1 PreLab Ngspice code

#### 3.1.1 Dark light

```
*solar cell under dark condition
.include Solar_Cell.txt
Vin 1 0 0
x1 1 2 solar_cell
vdiode 2 3 0
r 3 0 100
.dc Vin -2 2 0.0001
.control
run
let V_ = v(1)-v(2)
let power = (v(1)-v(2))*i(vdiode)
plot i(vdiode) vs v(1)-v(2)    power vs v(1)-v(2)
.endc
.end
```

#### 3.1.2 Light illumination of 8mA

```
*solar cell for illumination 8mA
.include Solar_Cell_8.txt
```

```

Vin 1 0 0
x1 1 2 solar_cell
vdummy 2 3 0
r 3 0 100
.dc Vin -2 2 0.0001
.control
run
let V_ = v(1)-v(2)
let power = (v(1)-v(2))*i(vdummy)
let dybydx=deriv(power)
plot i(vdummy) vs v(1)-v(2)    power vs v(1)-v(2)
meas dc isc find i(vdummy) WHEN V_=0
meas dc voc find V_ WHEN i(vdummy)=0
meas dc imp FIND i(vdummy) WHEN dybydx=0 cross=1
meas dc Vmp FIND V_ WHEN dybydx=0 cross=1
let fill_factor = imp*Vmp/(isc*vsc)
print fill_factor
.endc
.end

```

### 3.1.3 For light illumination of 10mA


```


```
*prelab of solar cell for illumination 10mA
.include Solar_Cell_10.txt
Vin 1 0 0
x1 1 2 solar_cell
vdummy 2 3 0
r 3 0 100
.dc Vin -2 2 0.0001
.control
run
let V_ = v(1)-v(2)
let power = (v(1)-v(2))*i(vdummy)
let dybydx=deriv(power)
plot i(vdummy) vs v(1)-v(2)    power vs v(1)-v(2)
meas dc isc find i(vdummy) WHEN V_=0
meas dc voc find V_ WHEN i(vdummy)=0
meas dc imp FIND i(vdummy) WHEN dybydx=0 cross=1
meas dc Vmp FIND V_ WHEN dybydx=0 cross=1
let fill_factor = imp*Vmp/(isc*vsc)
print fill_factor

.endc
.end
```


```

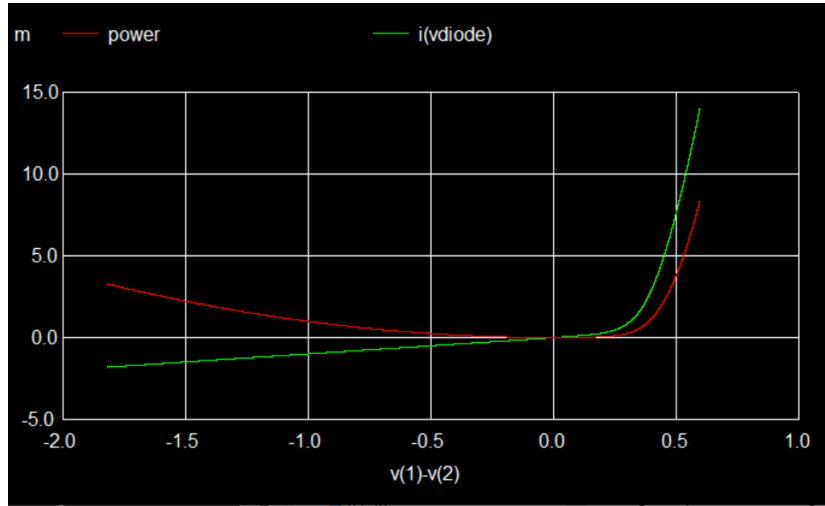
### 3.2 Simulation results for Dark, $I_1$ and $I_2$ respectively



```
ngspice 36
No compatibility mode selected!


Circuit: *prelab of solar cell under dark condition
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

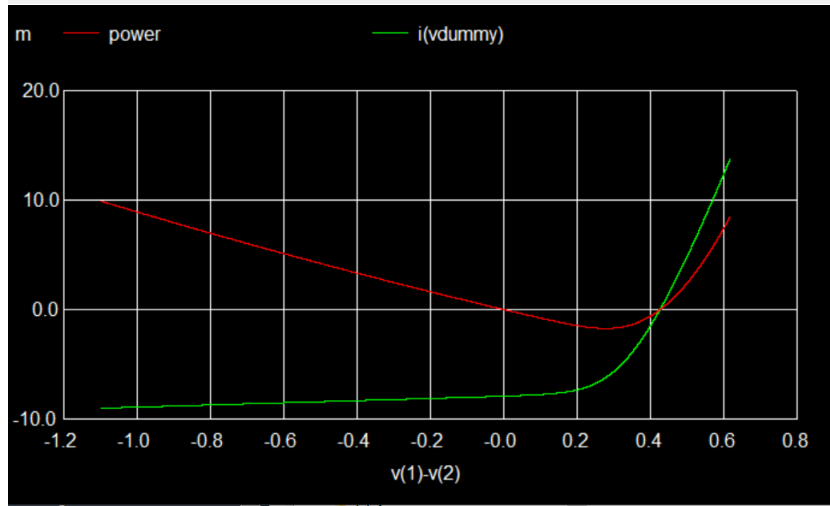No. of Data Rows : 40001
ngspice 10 ->
```



```
ngspice 36
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

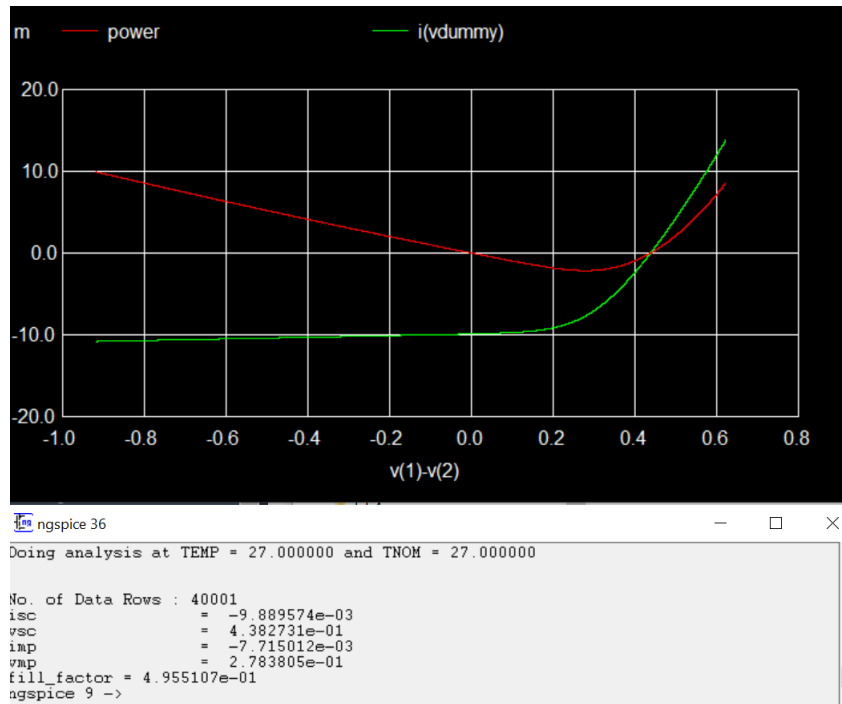
No. of Data Rows : 40001
isc          = -7.913629e-03
vsc          = 4.262215e-01
imp          = -6.222370e-03
vmp          = 2.780933e-01
fill_factor = 5.130212e-01
ngspice 7 ->
```




## 4 Experimental results

### 4.1 Experimental graph obtained from values taken in lab

#### 4.1.1 Dark condition

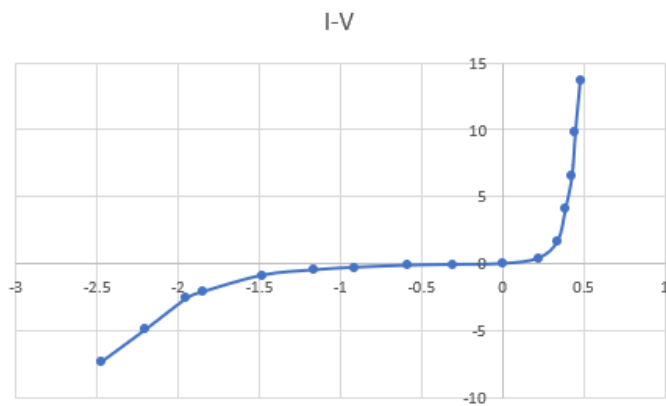

#### 4.1.2 Under $I_1$ illumination

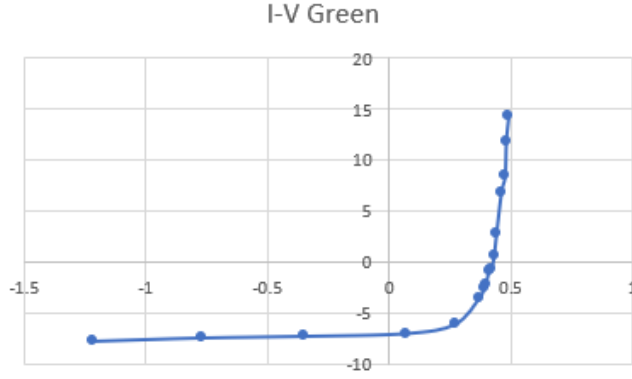

#### 4.1.3 Under $I_2$ illumination

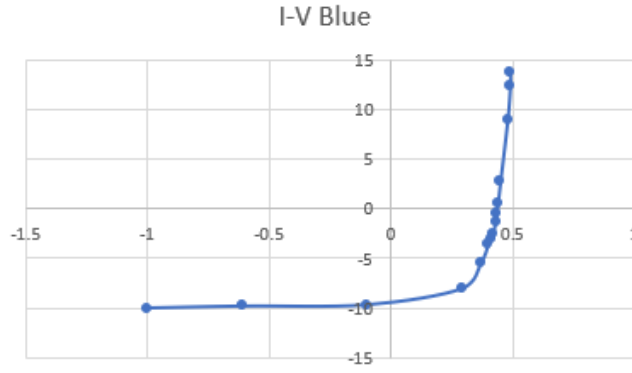


Table 1:  $I_{MP}, V_{MP}, I_{sc}, V_{oc}$  values


Illumination	$I_{MP}$	$V_{MP}$	$I_{sc}$	$V_{oc}$
$I_1 = 8mA$ simulation	$-6.23mA$	$0.27V$	$-7.88mA$	$0.43V$
$I_1 = 8mA$ <b>experimental</b>	$-6.27mA$	$0.31V$	$-10.87$	$0.45V$
$I_1 = 10mA$ simulation	$-7.72mA$	$0.29V$	$-9.86mA$	$0.44V$
$I_1 = 10mA$ <b>experimental</b>	$-8.45mA$	$0.30V$	$-10.86mA$	$0.46$

Table 2: Fill factor under illumination  $I_1$  and  $I_2$


Illumination	Exp. fillfactor	simulation fillfactor
$I_1 = 8mA$	0.397	0.496
$I_2 = 10mA$	0.507	0.516

## 4.2 Part-2 : Solar cell as power source

### 4.2.1 Under $I_1$ illumination

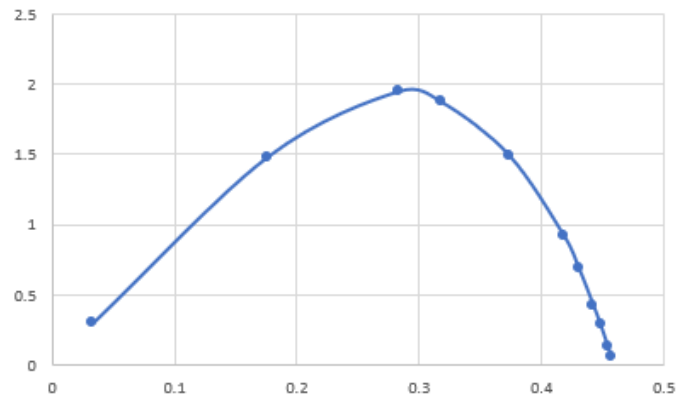


### 4.2.2 Under $I_2$ illumination

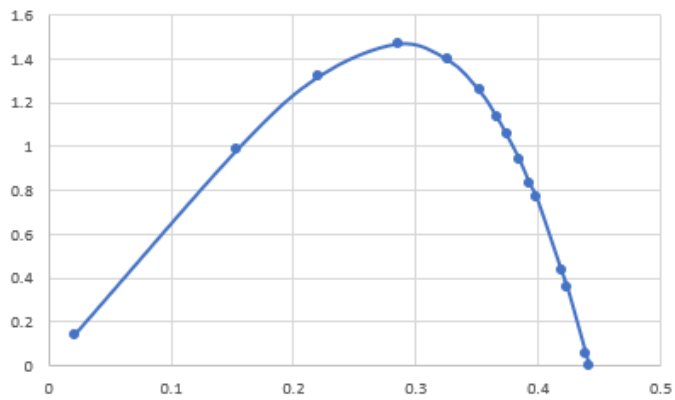




### 4.2.3 Superimposing the readings of part 1 and part 2

- For  $I_1$  illumination

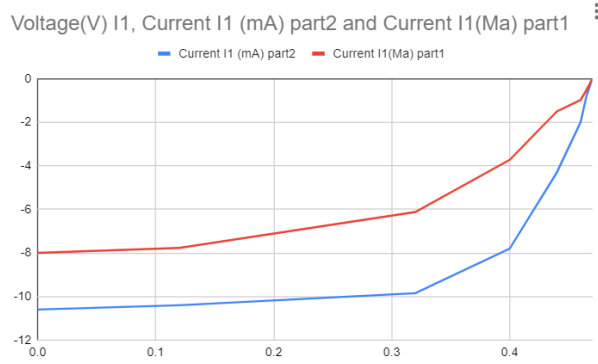


- For  $I_2$  illumination

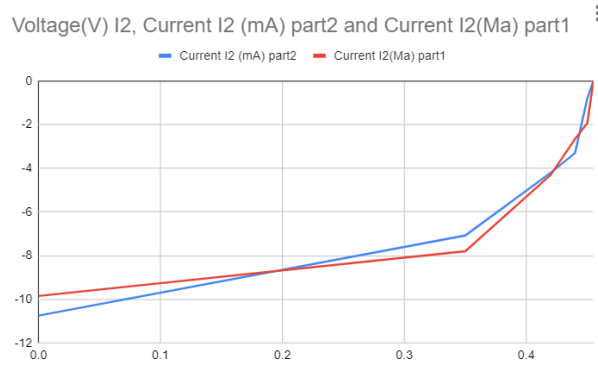


### 4.3 Part:-3 Measurement of $V_{oc}$ and $I_{sc}$ at different illumination levels for BLUE terminal illumination

- $I_{sc}$  vs  $I_{LED}$

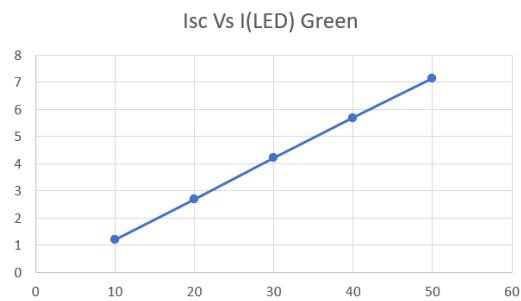

- $V_{oc}$  vs  $\log(I_{LED})$

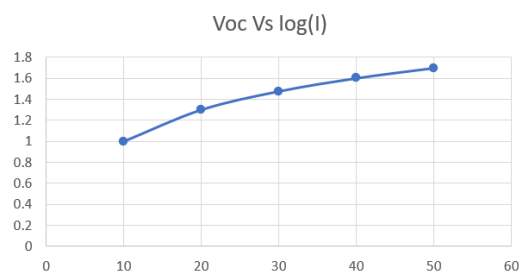

## 5 Experiment completion status

I have completed all the parts of the experiments in the report and did all the calculation which were told to do in the experiment.